



Faculty of Engineering and Technology
Electrical and Computer Engineering Department
ENEE2103
Circuits and Electronics Lab

Experiment No.4 - Pre Lab No.3
Sinusoidal Steady State Circuit Analysis

Student's Name: Lojain Abdalrazaq. **ID Number:** 1190707.

Instructor's Name: Dr. Ali Abdo.
Teaching assistant: Eng. Ismail Abualia.

Section: 5.

Apr 1, 2022

Table of Content:

1. Impedance.....	3
2. Capacitive and inductive behavior.....	9
3. Sinusoidal steady state power.....	13

1. Impedance:

- ✓ Connecting the first circuit using PSpice:

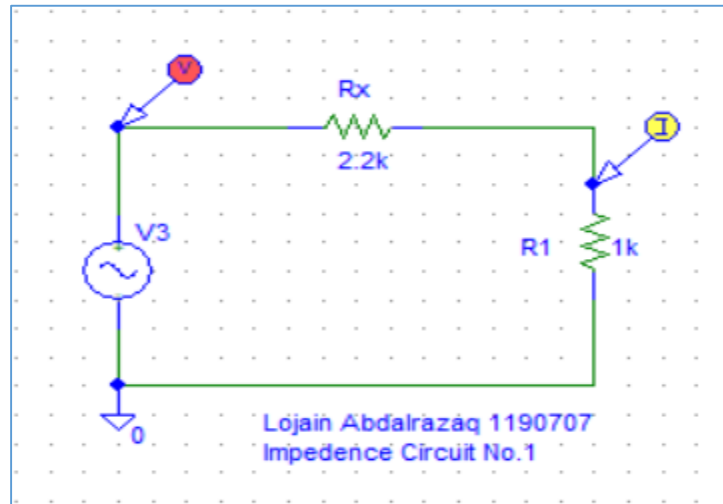


Fig1.1: Connecting the circuit using PSpice.

- ✓ Calculating the total impedance using the total voltage and current:

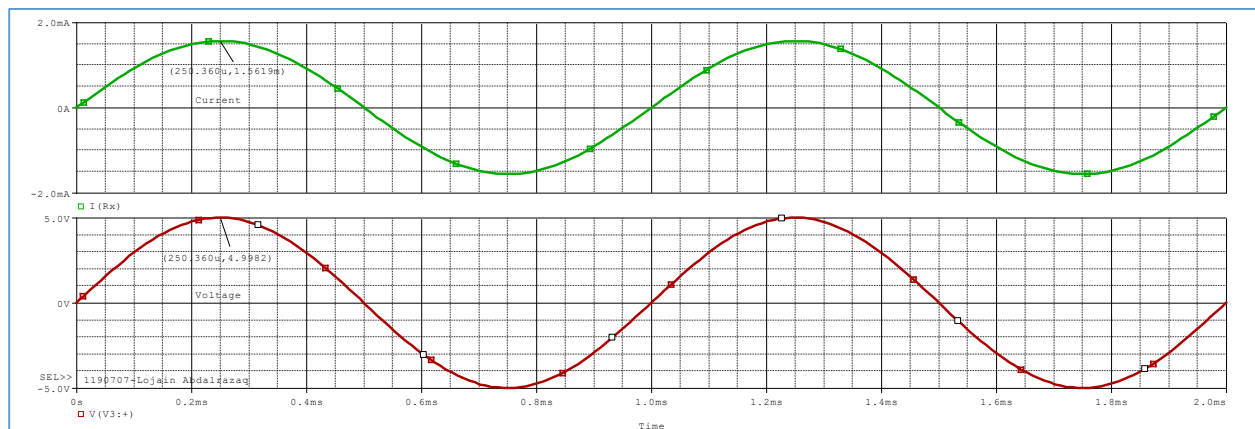


Fig1.2: Current and voltage through the circuit(Freq =1kHz).

In the first circuit, $Z=R$ because the circuit has resistors only.
from $V=RI \Rightarrow V=ZI \therefore Z = \frac{V}{I} = \frac{4.998}{1.5619m} = 3.1999 k\Omega$
And theoretically:- $Z=R_{eq} = 1k + 2.2k = 3.2k\Omega$, too close!!

Fig1.3: Calculating the total impedance.

✓ Repeating the previous steps with 500 Hz , 1500 Hz:

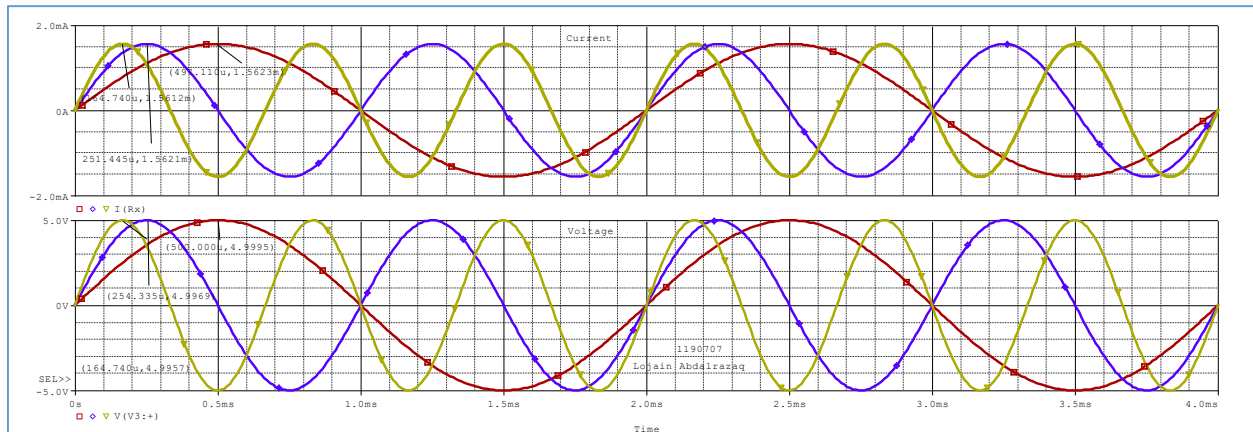


Fig1.4: Current and voltage through the circuit when Freq=1kHz,1.5kHz and 0.5kHz.

Note:

From the previous figure, we notice that the total impedance will be almost equal **3.199K**, and **3.2K** theoretically and there is no phase shift (Equals to 0).

✓ Connecting the RC using PSpice and measuring the total Impedance:

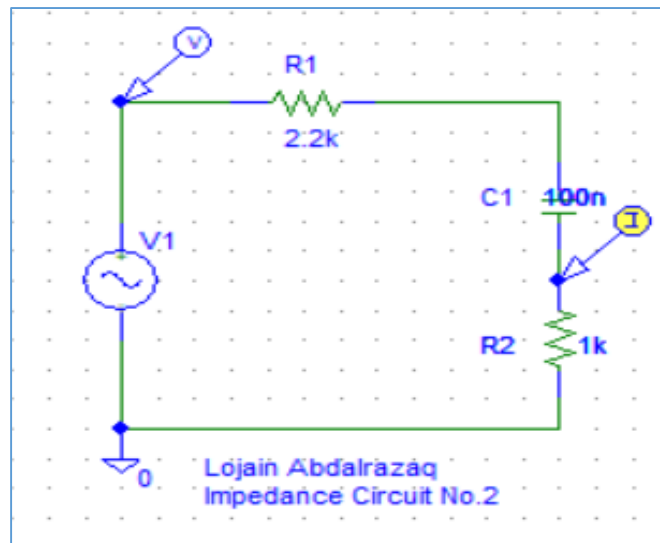


Fig1.5: Connecting the RC circuit using PSpice.

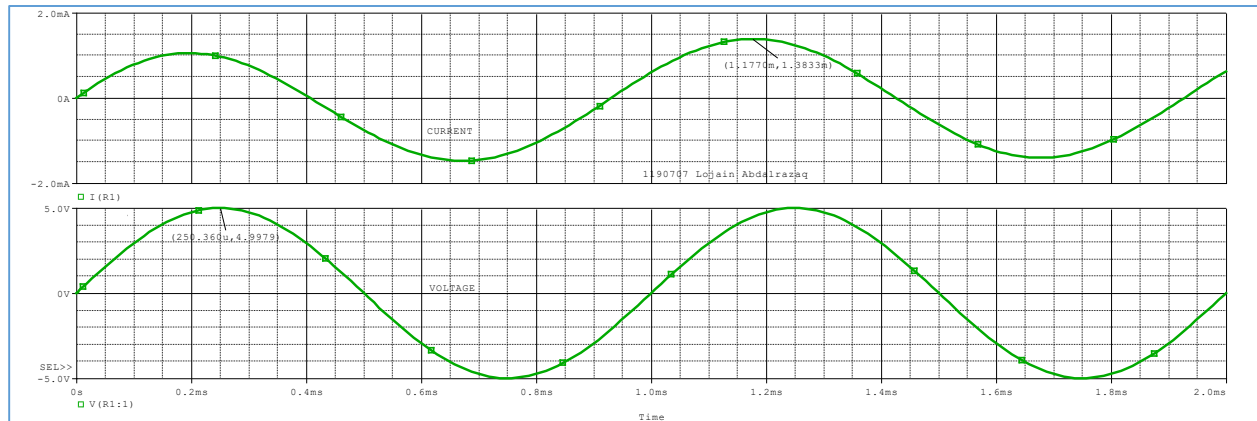


Fig1.6: Voltage and current through the RC circuit when Freq=1kHz.

⇒ RC Circuit:-

From the graph, we can find that $V_{max} = 4.997 \text{ V}$ and $I_{max} = 1.383 \text{ mA}$

$$\therefore Z = \frac{V_{max}}{I_{max}} = \frac{4.997}{1.383 \text{ mA}} = 3.613 \text{ k}\Omega$$

$$\therefore \text{Phase-Shift} = \left(\frac{1.1770 \text{ ms} - 1.2504 \text{ ms}}{\text{Period} \Rightarrow 1 \text{ ms}} \right) * 360 = -26.424 \text{ deg.}$$

Theoretically :- $Z = R_{eq} + \frac{1}{j\omega C} = 2.2\text{k} + 1\text{k} + \frac{1}{j(2\pi)(1\text{k})(100\text{n})} = 3.2\text{k} + 1.59(-j)\text{k}$

Z as magnitude : $|Z| = \sqrt{(3.2)^2 + (1.59)^2} = 3.573 \text{ k}\Omega$

phase = $\tan^{-1} \frac{y}{x} = \tan^{-1} \left(\frac{-1.59\text{k}}{3.2\text{k}} \right) = -26.4216 \text{ deg}$

Note: the results are too close!!

Fig1.7: Calculating the total impedance for the RC circuit.

✓ Repeating the previous steps with signal frequencies: 500Hz , 1500 Hz:

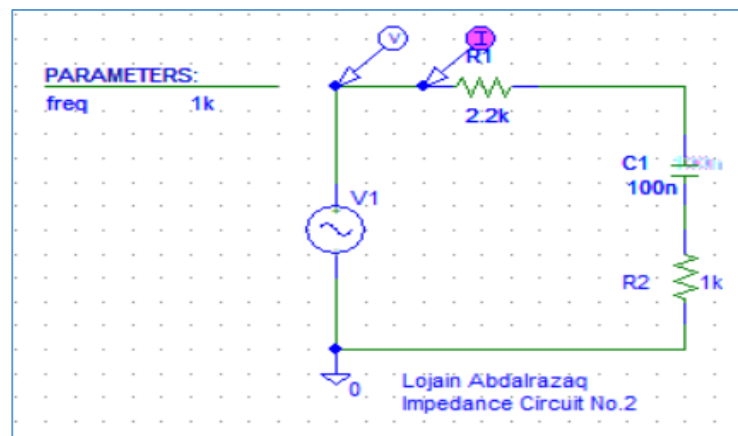


Fig1.8: Connecting the RC circuit with different frequencies.

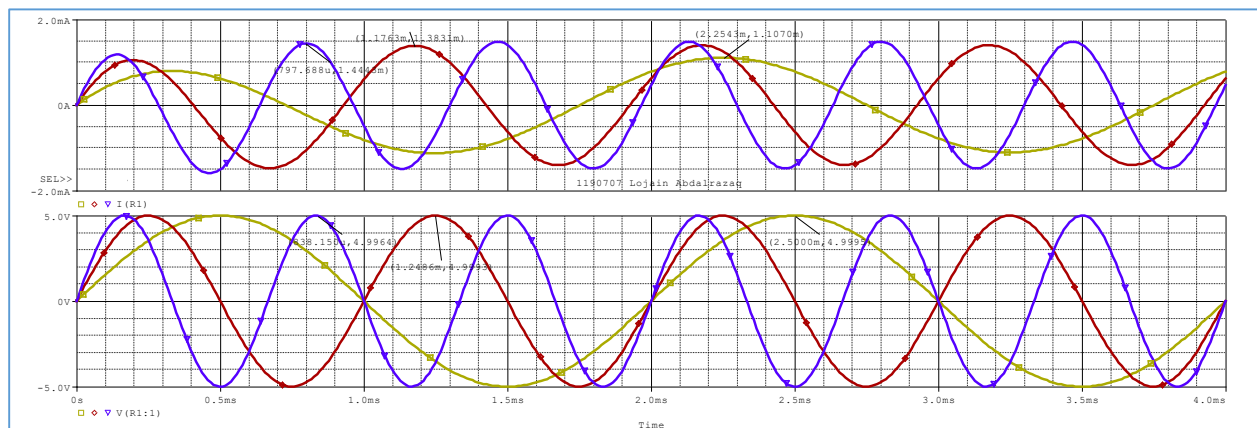


Fig1.8: Current and voltage through the RC circuit when Freq=1kHz, 1.5kHz and 0.5kHz.

⇒ When Frequency = 1.5kHz:

From the graph, we can notice that $V_{max} = 4.9964V$ and $I_{max} = 1.4443mA$

$$* Z_{max} = \frac{V_{max}}{I_{max}} = \frac{4.9964}{1.4443mA} = 3.459k\Omega$$

$$* \text{Phase} = \frac{(0.797688m - 0.83815m) \times 360}{0.6666m} = -21.849 \text{ deg}$$

$$\text{Theor.} \therefore Z = R_{eq} + \frac{1}{j\omega C} = 3.2k + \frac{1}{j(2\pi \cdot 1.5k)C} = 3.2 - j1.06k\Omega$$

$$Z \text{ as magnitude} \Rightarrow \sqrt{3.2^2 + 1.06^2} = 3.37099k\Omega$$

$$Z \text{ as phase} \Rightarrow \tan^{-1} \frac{y}{x} = \tan^{-1} \left(\frac{-1.06}{3.2} \right) = -18.327 \text{ deg}$$

⇒ When Frequency = 0.5kHz:

From the graph, we can find that $V_{max} = 4.9995V$ and $I_{max} = 1.1070mA$

$$* Z = \frac{V_{max}}{I_{max}} = \frac{4.9995}{1.1070mA} = 4.5162k\Omega$$

$$* \text{Phase shift} = \frac{(2.2543m - 2.5m) \times 360}{2m} = -44.226 \text{ deg}$$

$$\text{Theoretically: } Z = R_{eq} + \frac{1}{j\omega C} = 3.2k - j(3.183)k\Omega$$

$$Z \text{ as magnitude} \therefore |Z| = \sqrt{(3.2)^2 + (3.18)^2} = 4.5113k\Omega$$

$$\text{Phase} = \tan^{-1} \frac{y}{x} = \tan^{-1} \left(\frac{-3.183k}{3.2k} \right) = -44.847^\circ$$

✓ **Connecting the RL using PSpice and measuring the total Impedance:**

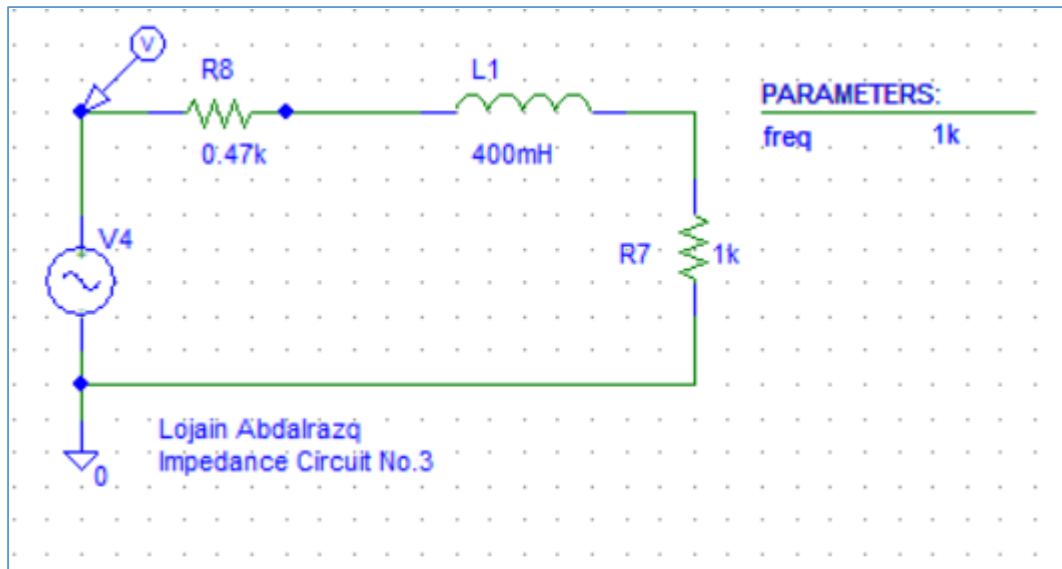


Fig1.9: Connecting the RL circuit using PSpice.

✓ **Calculating the total impedance using the total voltage and current:**

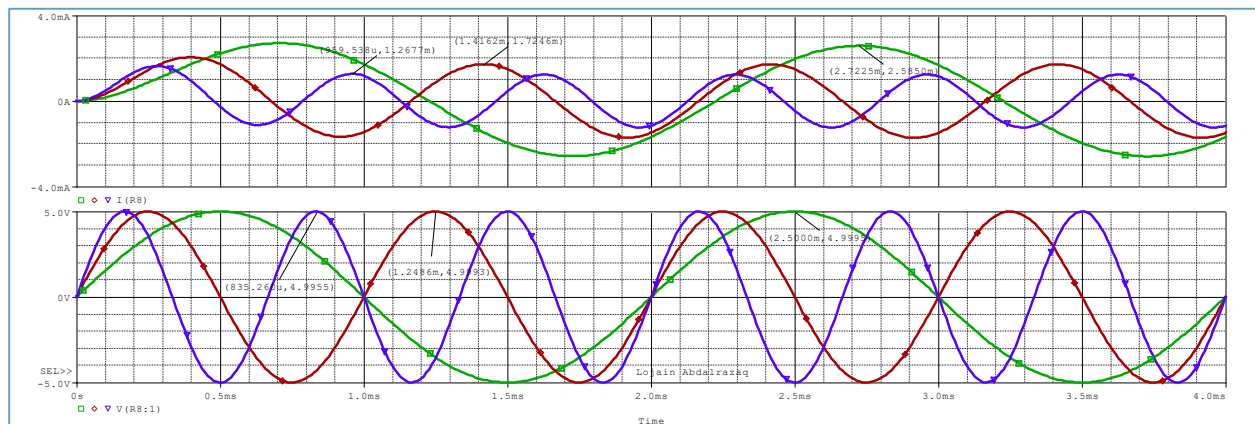



Fig1.10: Current and voltage through the RL circuit when $Freq=1kHz, 1.5kHz$ and $0.5kHz$.

⇒ RL Circuit:

When Frequency = 1000 Hz

$$* Z = \frac{V_{max}}{I_{max}} = \frac{4.9993 \text{ V}}{1.7246 \text{ m}} = 2.8988 \text{ k}\Omega$$
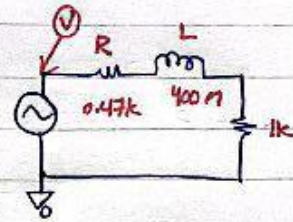
$$* \text{Phase-Shift} = \frac{T \times 360}{(1/f)} = \frac{(1.4162 \text{ m} - 1.2486 \text{ m}) \times 360}{1 \times 10^{-3}} = 60.336 \text{ deg}$$



By theoretically: $* Z = R_{eq} + j\omega L = 1.47 + j(2.512) \text{ k}\Omega$
 $|Z| = \sqrt{1.47^2 + 2.512^2} = 2.905 \text{ k}\Omega$
 $\Delta\theta = \tan^{-1}\left(\frac{2.512}{1.47}\right) = 59.66 \text{ deg}$

When Frequency = 500 Hz

$$* Z = \frac{V_{max}}{I_{max}} = \frac{4.9995}{2.585 \text{ m}} = 1.93 \text{ k}\Omega$$

$$* \text{Phase-shift} = \frac{T \times 360}{\text{per}} = \frac{(2.7225 \text{ m} - 2.5 \text{ m}) \times 360}{2 \text{ ms}} = 40.05$$

By theoretically: $* Z = R_{eq} + j\omega L = 1.47 + j(2\pi \times 0.5 \text{ k})L = 1.47 + j1.257$
 $|Z| = \sqrt{1.47^2 + 1.257^2} = 1.934 \text{ k}\Omega$
 $\Delta\theta = \tan^{-1}\left(\frac{1.257}{1.47}\right) = 40.5 \text{ deg}$

When Frequency = 1500 Hz

$$* Z = \frac{V_{max}}{I_{max}} = \frac{4.9955 \text{ V}}{1.2677 \text{ m}} = 3.9406 \text{ k}\Omega$$

$$* \text{Phase-Shift} = \frac{T \times 360}{\text{per}} = \frac{(0.9595 \text{ m} - 0.8352 \text{ m}) \times 360}{0.666667} = 67.122 \text{ deg}$$

By theoretically: $* Z = R_{eq} + j\omega L = 1.47 \text{ k} + j3.77 \text{ k}\Omega$
 $|Z| = \sqrt{1.47^2 + 3.77^2} = 4.04 \text{ k}\Omega$
 $\Delta\theta = \tan^{-1}\left(\frac{3.77}{1.47}\right) = 68.9 \text{ deg}$

2. Capacitive and inductive behavior:

✓ Connecting the RLC using PSpice:

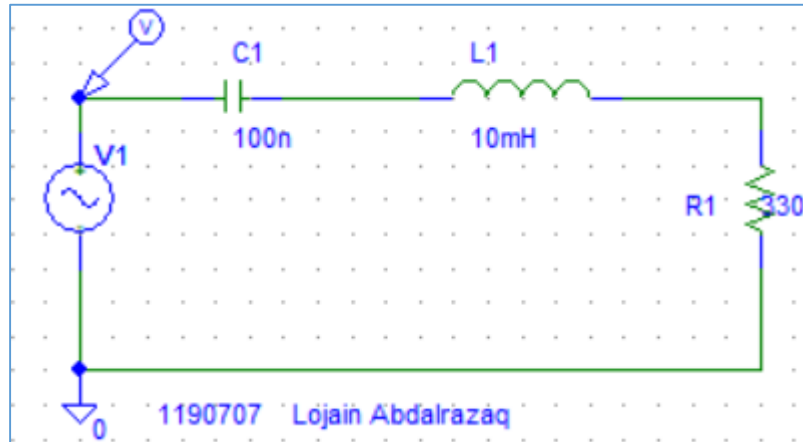


Fig1.11: Connecting the RCL circuit using PSpice.

✓ Measuring the phase shift between the total current and the source voltage:

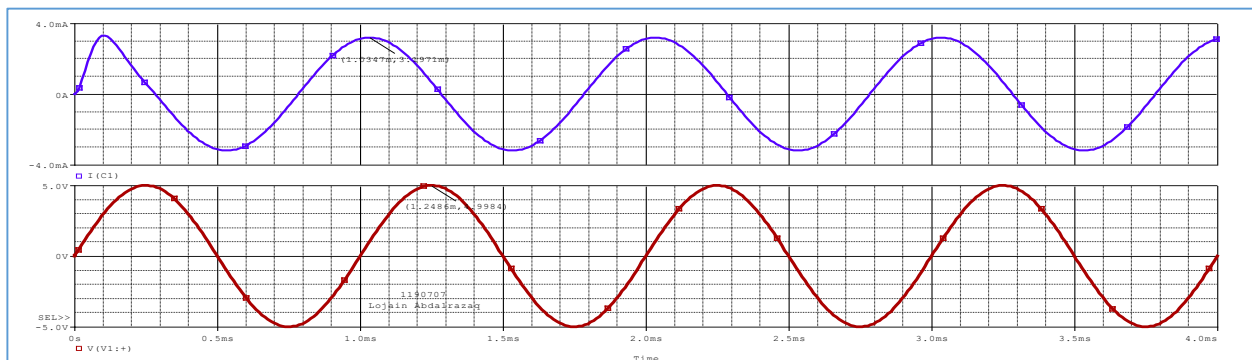


Fig1.12: Total voltage and current in RLC circuit when Freq=1000 Hz.

$$\Rightarrow \text{Using the graph, phase-shift} = \frac{(1.0347\text{m} - 1.2486\text{m}) \times 360}{1\text{m}} = -77.004^\circ$$

$$\Rightarrow \text{Theoretically: } Z = R_{eq} + j(2\pi fL) + \frac{-j}{2\pi fC} = 330 + -j1528.7$$

$$\therefore \text{Phase-Shift} = \tan^{-1}\left(\frac{y}{x}\right) = \tan^{-1}\left(\frac{-1528.7}{330}\right) = -77.82^\circ$$

$$\therefore \text{Because the shift is negative, that means the current leads the voltage by } 77.82^\circ$$

$$\therefore \text{the circuit is capacitive.}$$

✓ Calculating the resonance frequency and measuring the phase shift($F=F_{res}$):

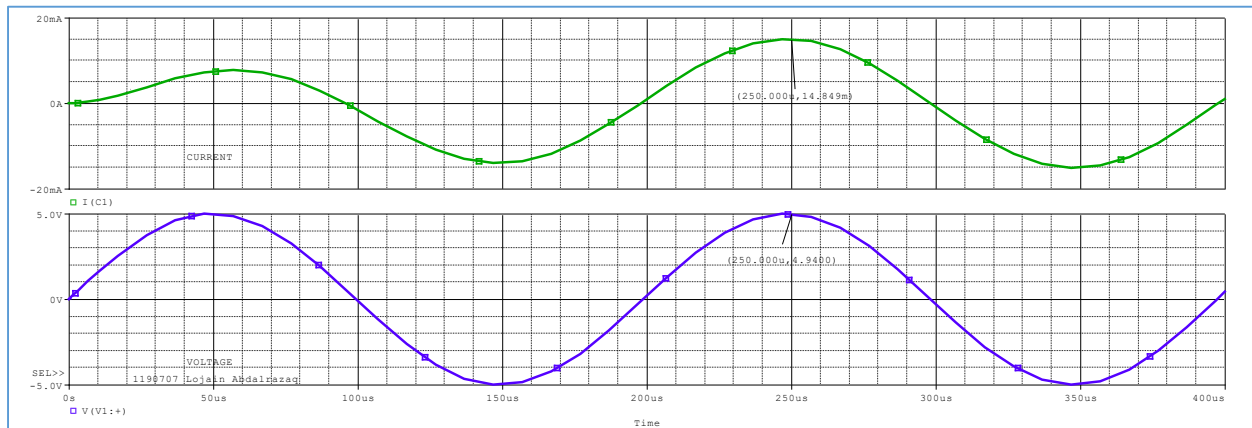


Fig1.13: Current and voltage through the RLC circuit when $F_{eq} = \text{resonance} = 5033\text{Hz}$.

$\Rightarrow \text{When } F = f_0$
 $* f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(10m)(100n)}} = 5033\text{ Hz}$
 $+ \text{Phase shift: using graph: } \frac{T \times 360}{\text{Per}} = 0 \text{ degree}$
 $\therefore \text{ calculation } \Rightarrow Z = j\omega L + \frac{1}{j\omega C} = \frac{1}{2\pi(5033)(100n)} + j(2\pi 5033) 10m$
 $\therefore \tan^{-1}\left(\frac{0}{330}\right) = 0 \text{ deg} = 0$

✓ Changing the source frequency to $2f_0$ and calculating the phase shift:

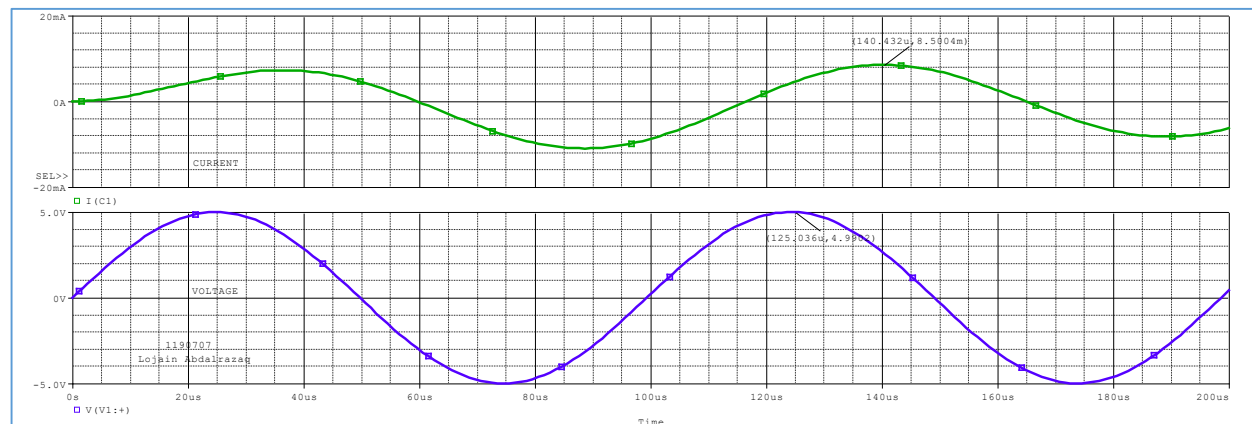


Fig1.13: Current and voltage through the RLC circuit when $F_{eq} = 2 * \text{resonance} = 10066\text{Hz}$.

According to the calculation, its inductive circuit:

⇒ When $F = 2F_{\text{res}}$:

* From graph ⇒ Phase-Shift = $\frac{(140.432\mu - 125.036\mu) 360}{99.344\mu} = 55.79 \text{ deg}$

* From calculation ⇒ $Z = R_{\text{eq}} + \underbrace{\left(\frac{1}{j\omega C} \right)}_{\text{complex}} + j\omega L = j 474.35$

∴ Phase-Shift ⇒ $\tan^{-1}\left(\frac{y}{x}\right) = \tan^{-1}\left(\frac{474.35}{330\Omega}\right) = 55.17 \text{ deg}$

✓ Doubling the value of capacitor:

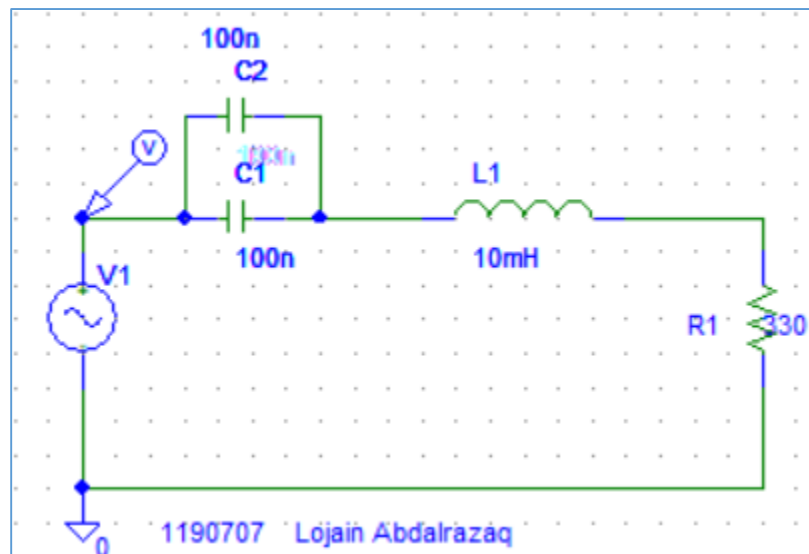


Fig1.14: Connecting the RCL circuit with doubling the capacitor.

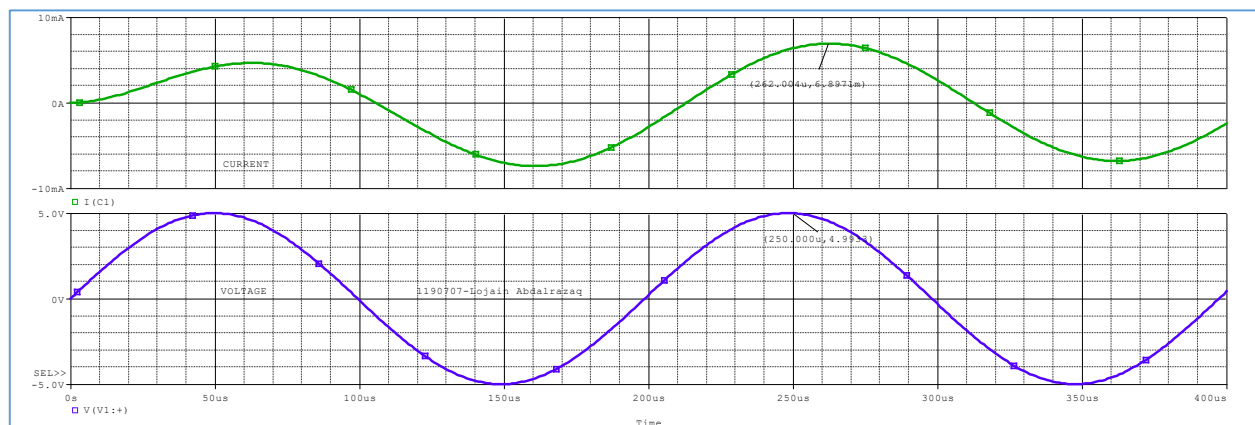


Fig1.15: Current and voltage through the RLC circuit when DOUBLING the capacitor.

✓ Doubling the value of inductor:

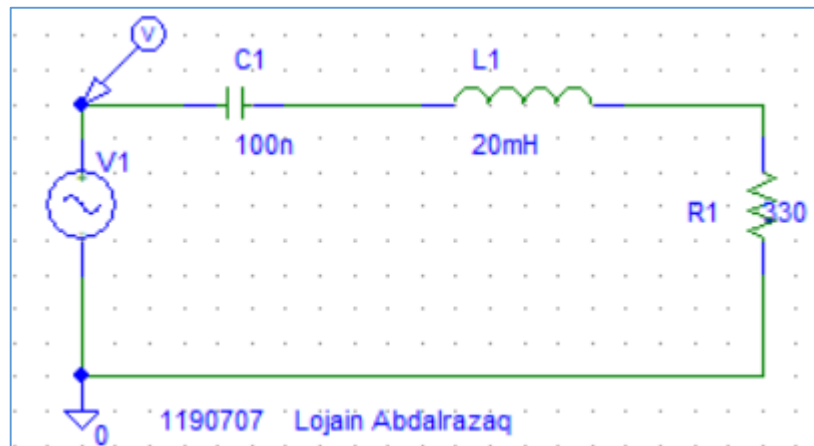


Fig1.16: Connecting the RCL circuit with doubling the inductor.

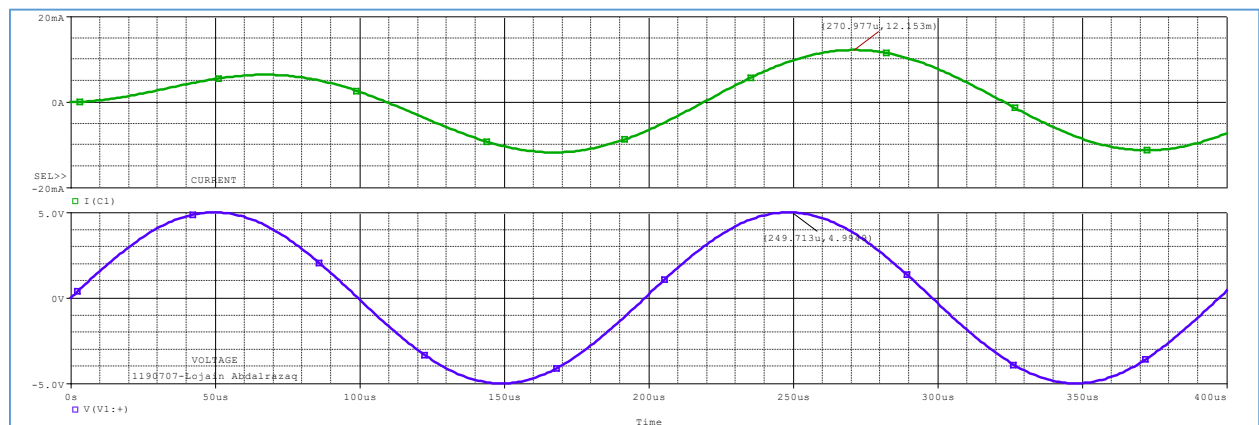


Fig1.17: Current and voltage through the RLC circuit when DOUBLING the inductor.

✓ Calculations when doubling the capacitor and the inductor:

⇒ When doubling the capacitor and inductor:

1] Doubling the capacitor:

* From graph: Phase-shift = $\frac{(262.004\mu - 250.4) \times 360}{198.68\mu} = 21.74 \text{ deg}$

* From calculation: $X = j\omega L + \frac{1}{j\omega C} = j(158.122)$

∴ Phase-shift = $-\tan^{-1}\left(\frac{158.122}{330}\right) = 25.6 \text{ deg}$

2] Doubling the inductor:

* From graph: Phase-shift = $\frac{(270.977\mu - 249.713\mu) \times 360}{198.689\mu} = 38.527 \text{ deg}$

* From calculation: $X = j\omega L + \frac{1}{j\omega C} = j(316.233)$

∴ Phase-shift = $-\tan^{-1}\left(\frac{316.233}{330}\right) = 43.78^\circ$

3. Sinoidal steady state power:

✓ Connecting the circuit using PSpice:

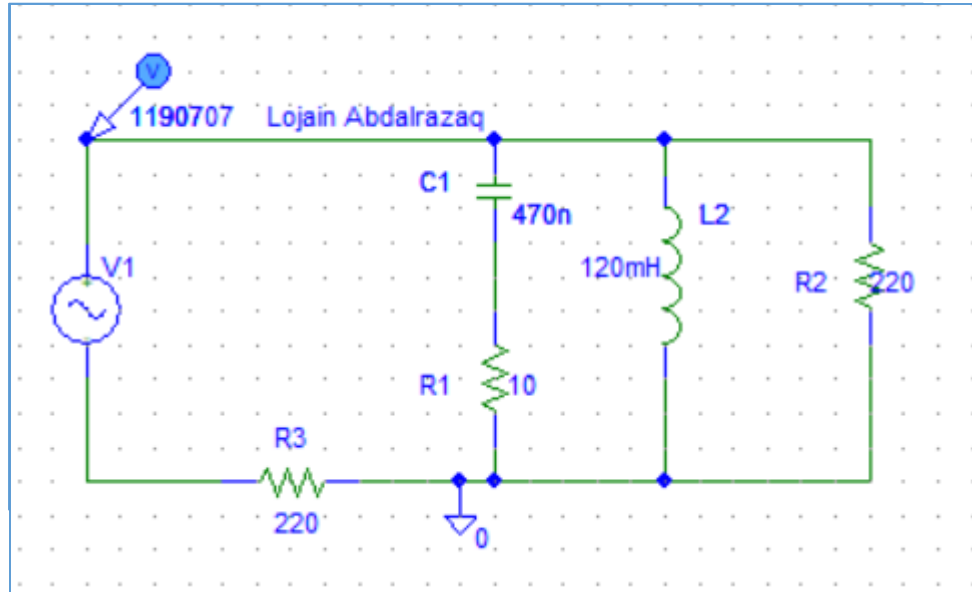


Fig1.18: Connecting the circuit using PSpice.

✓ Plotting current and voltage across R1:

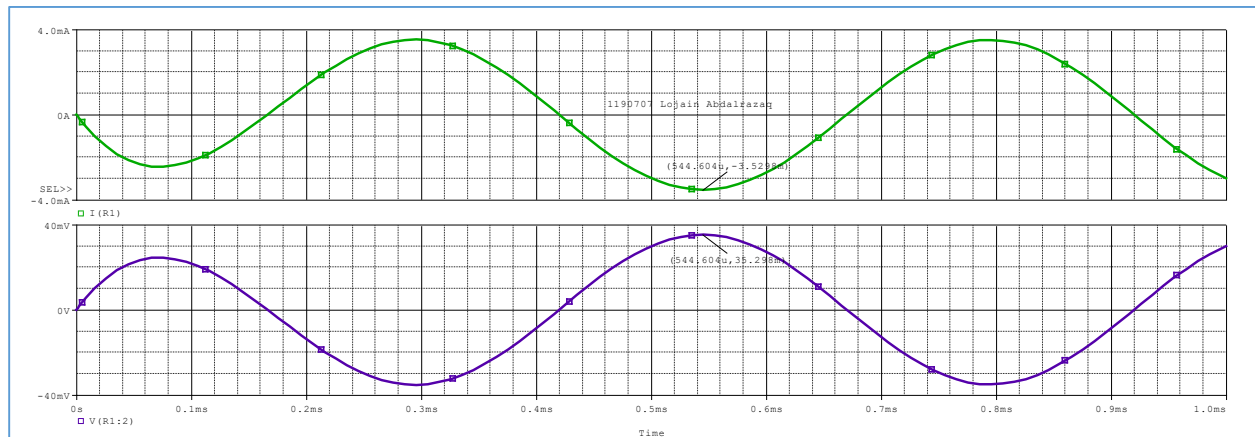


Fig1.19: Current and voltage across R1.

✓ **Plotting V_s and I_s :**

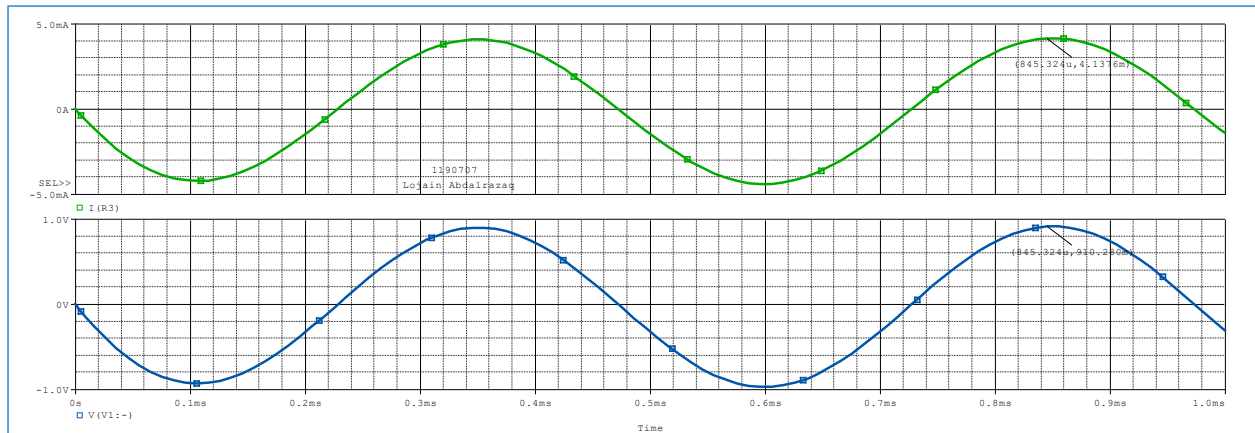


Fig1.19: plot of V_s and I_s .

✓ **Plotting V_c and I_c :**

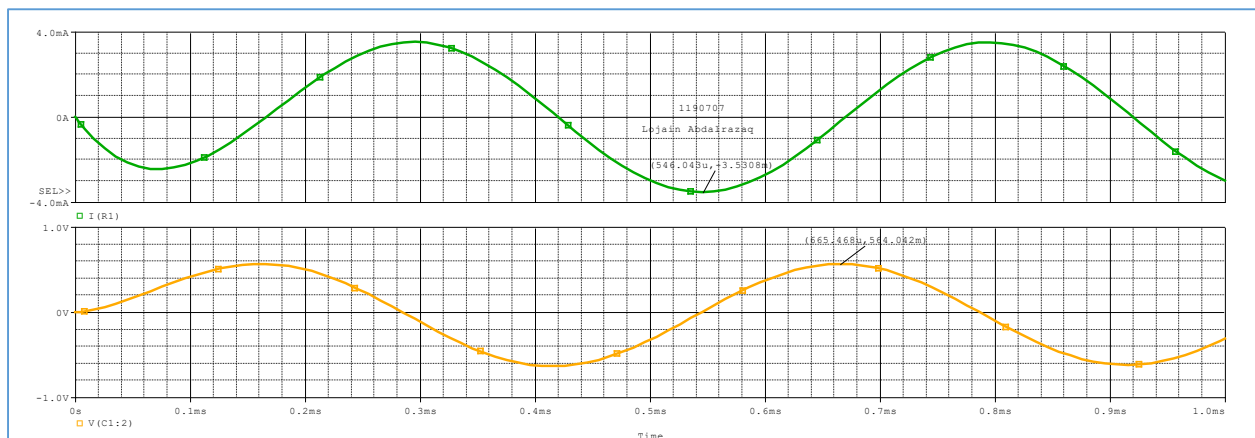


Fig1.20: plot of V_c and I_c .

✓ **Plotting V_L and I_L :**


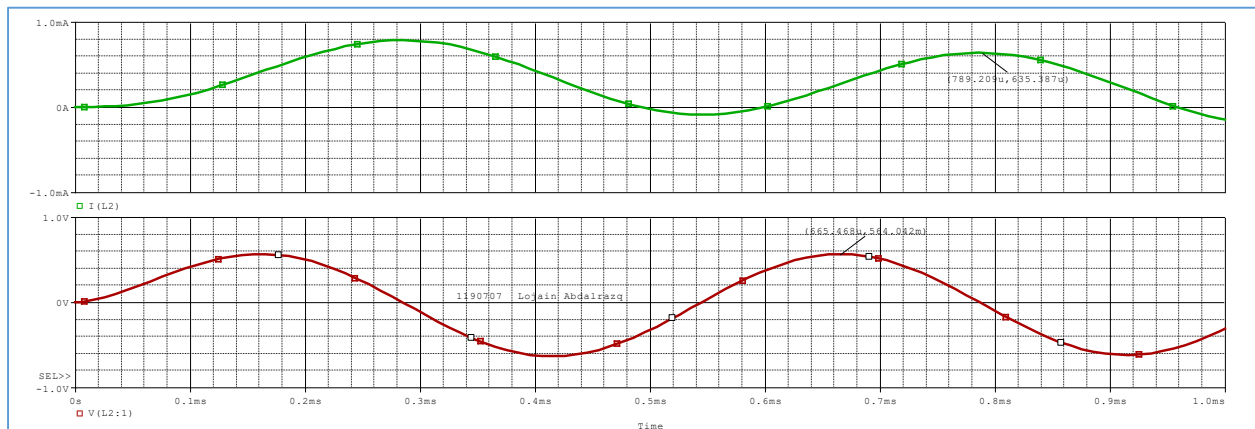


Fig1.21: plot of V_L and I_L .

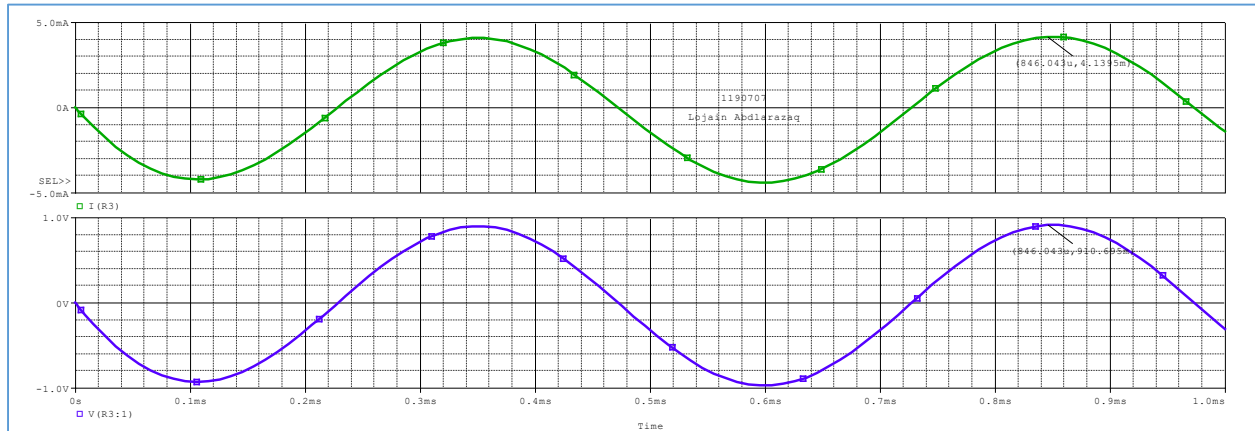✓ Plotting voltage across R3=220 ohm and Is:



✓ Phase Shift calculations:

* Phase-shift of V_s and I_s : Note: $V_{rms} = V_P / \sqrt{2} \Rightarrow V_P = 1.4142V$
 using the graph $\Rightarrow \frac{(845.324u - 845.324u) * 360}{0.5m} = \boxed{0}$

* Phase-Shift of V_L and I_L :
 using the graph $\Rightarrow \frac{(546.043u - 665.468u) * 360}{\text{Period}} = \boxed{-85.96}$

* Phase-Shift of V_L and I_L :
 using the graph $\Rightarrow \frac{(789.209u - 665.468u) * 360}{0.5m} = \boxed{87.1^\circ}$

* Phase-Shift of $V_{R=220}$ and I_s : $\frac{(846.043u - 846.043u) * 360}{0.5m} = \boxed{0}$