



Faculty of Engineering and Technology
Electrical and Computer Engineering Department

ENEE2103

Circuits and Electronics Lab

Experiment No.3 - Pre Lab No.2

First and Second Order Circuits

Student's Name: Lojain Abdalrazaq. **ID Number:** 1190707.

Instructor's Name: Dr. Ali Abdo.

Teaching assistant: Eng. Ismail Abualia.

Section: 5.

March 25, 2022

Table of Content

1. Part A: RC Circuit.....	2
2. Part B: RL Circuit.....	5
3. Part C: RLC Circuit.....	10

1. Part A: RC Circuit

- **RC Circuit simulation using PSpice software:**

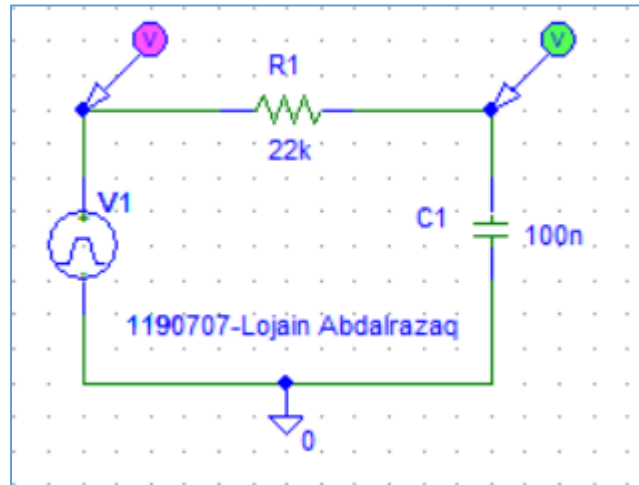


Fig1.1: Circuit simulation using Pspice.

- **Plotting the voltage across the capacitor:**

The following figure shows the voltage across the capacitor (charging and discharging) and the pulse voltage source:

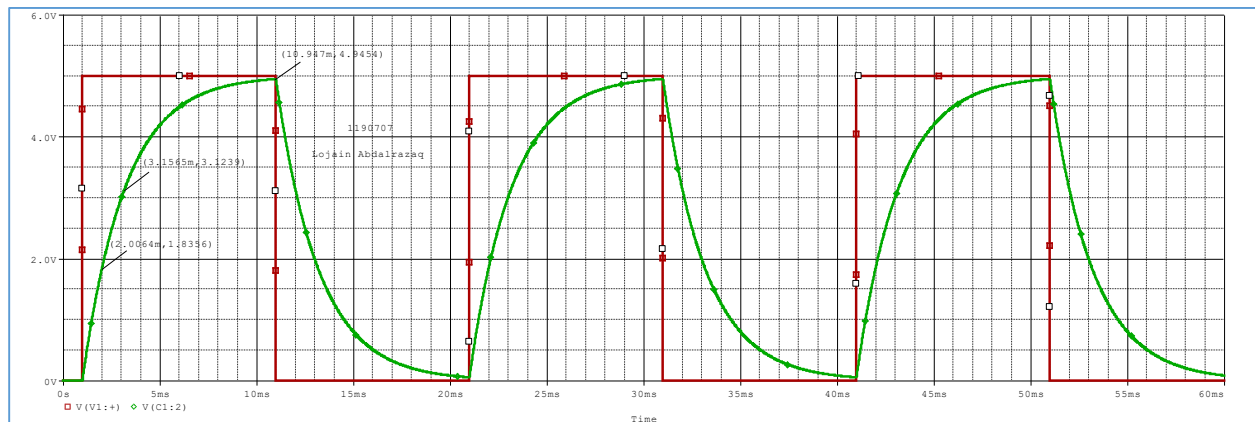


Fig1.2: The voltage across the capacitor.

- **RC Circuit Calculations:**

From the previous plot, we can find and measure the value of the **V_{max}** and **time constant** using the plotting in PSpice software and theoretically, and results were **too close** as shown:

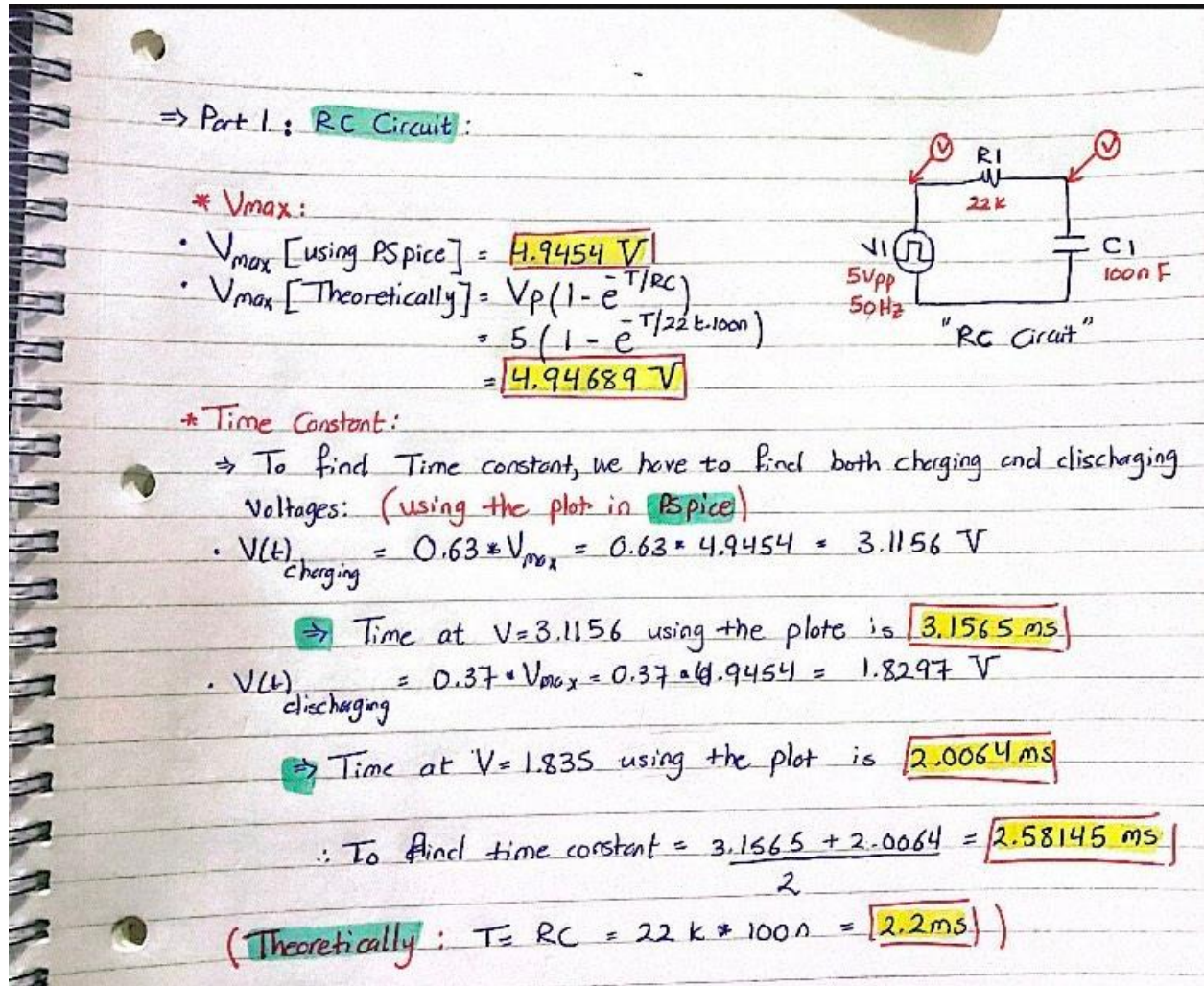


Fig1.3: Finding V_{max} and time constant using the plot in PSpice for the capacitor.

Also, to find the value of the capacitor using PSpice:

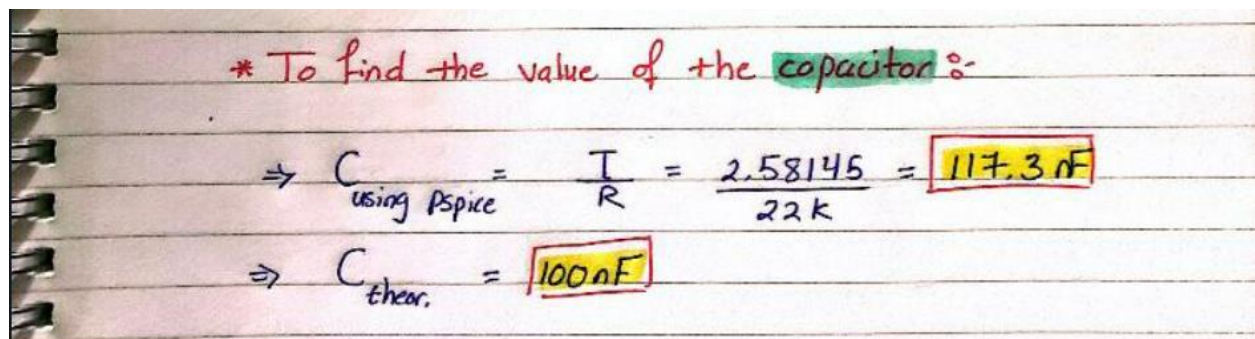


Fig1.4: Finding the capacitor value using PSpice results.

2. Part B: RL Circuit

- **RL Circuit simulation using PSpice software:**

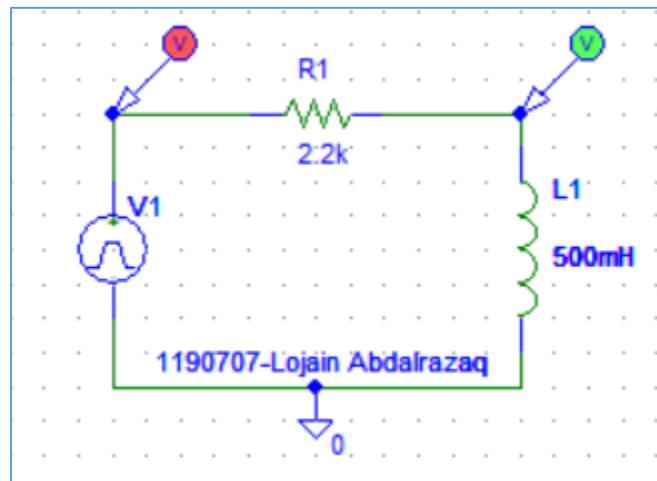


Fig1.5: Circuit simulation using PSpice when $f=500\text{Hz}$.

- **Plotting the voltage across the inductor:**

The following figure shows the voltage across the inductor when the $f=500\text{Hz}$ and $V_{p-p}=10\text{V}$.

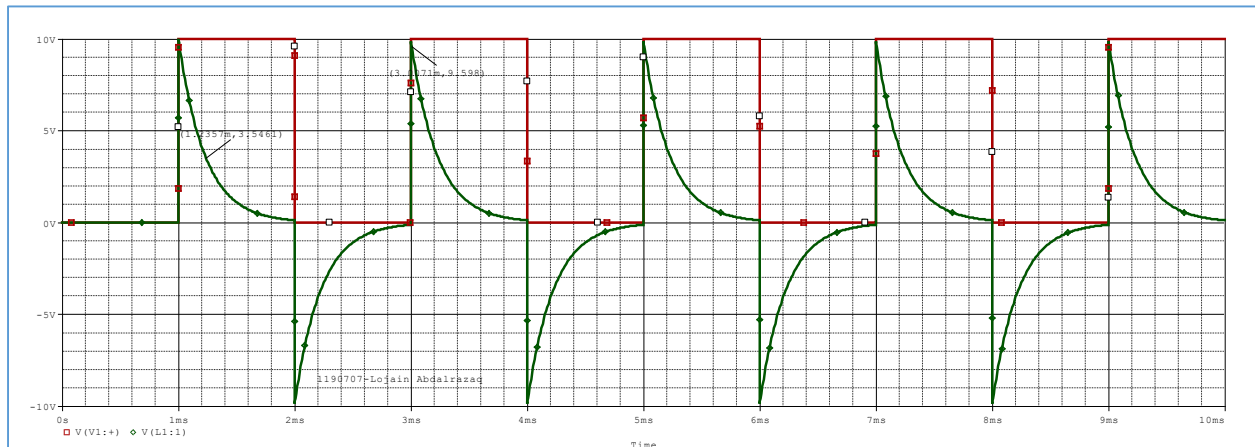


Fig1.6: The voltage response of the inductor.

- ✓ From the figure(1.6), which is the voltage response of the inductor, we can find the value of **V_{max}** and **time constant**, the results was so close to the theoretical ones as shown in the following:

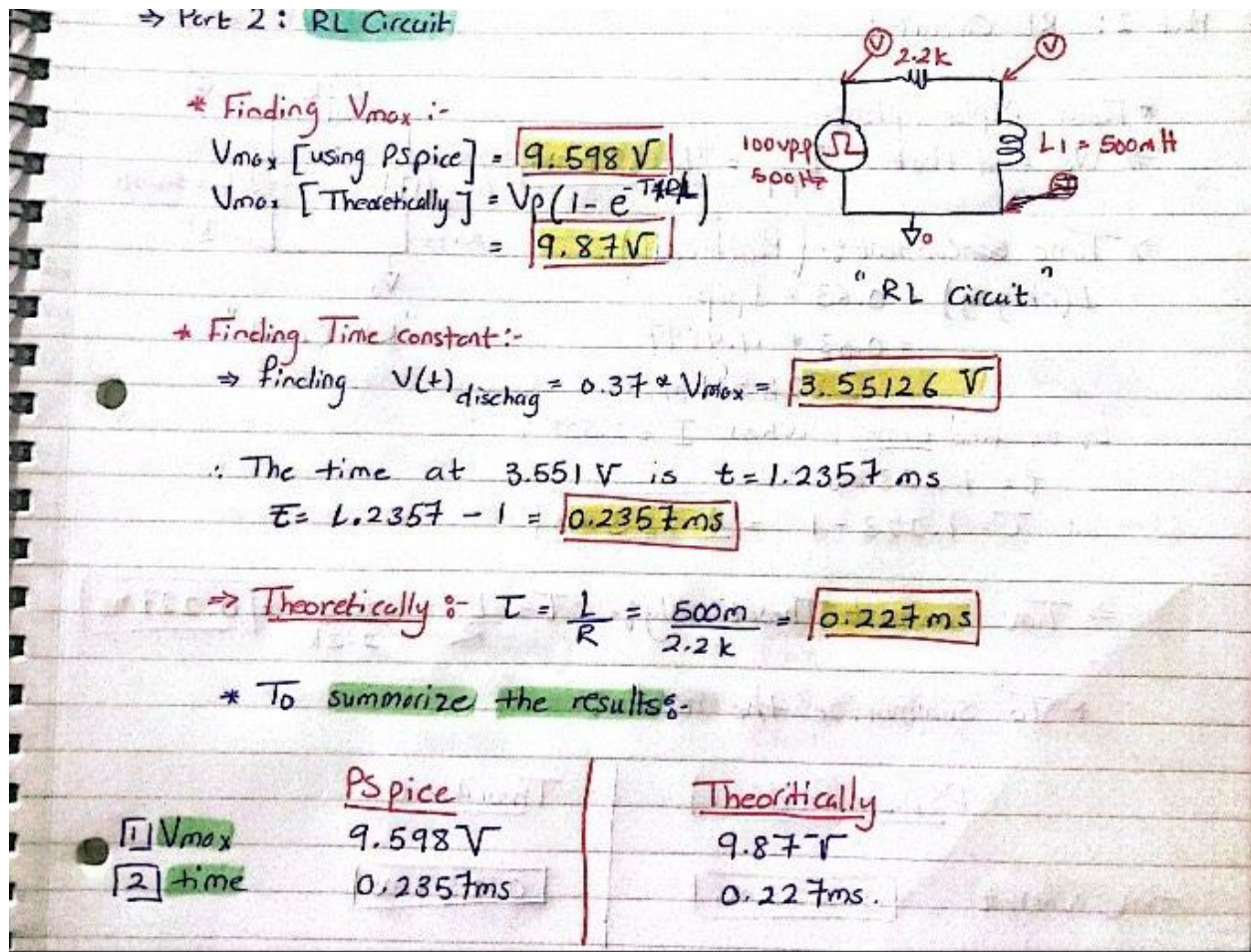


Fig1.7: Finding V_{max} and time constant using the plot of the voltage across the inductor.

- **RL Circuit simulation using PSpice software:**

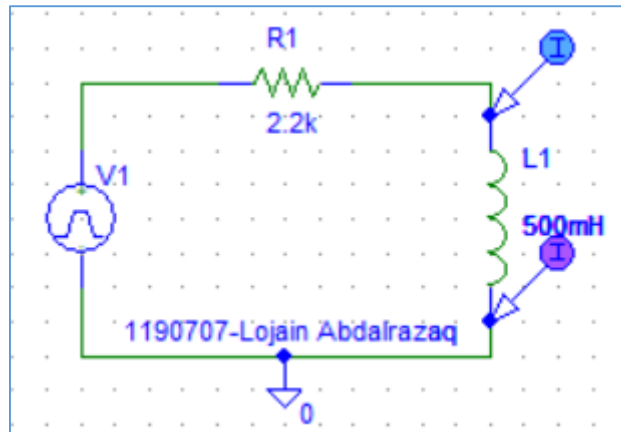


Fig1.8: Circuit simulation using PSpice when $f=500\text{Hz}$.

- **Plotting the current across the inductor:**

The following figure shows the current across the inductor when the $f=500\text{Hz}$ and $V_{p-p}=10\text{V}$.

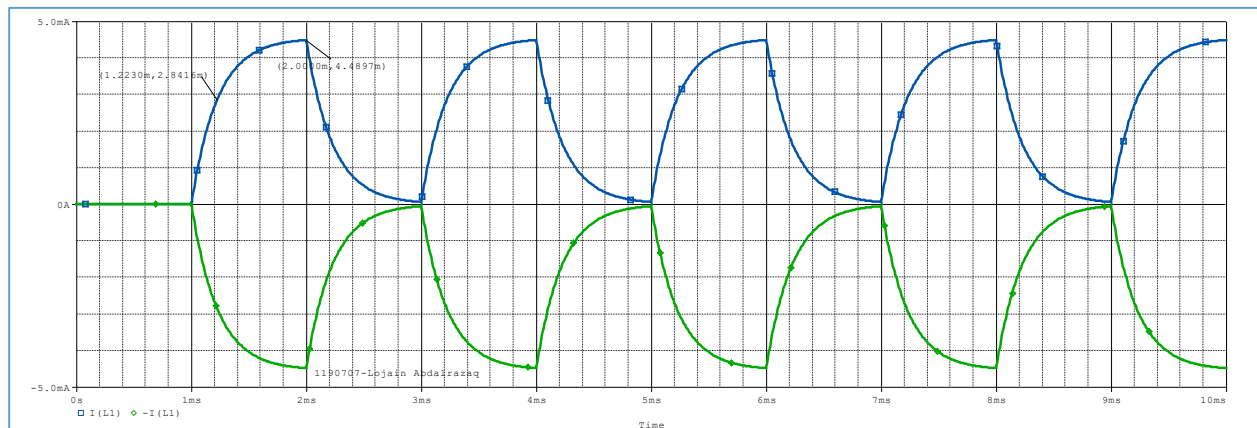


Fig1.9: The current response of the inductor.

- ✓ From the figure(1.9), which is the current response of the inductor, we can find the value of **time constant**, the results was so close to the theoretical ones as shown in the following:

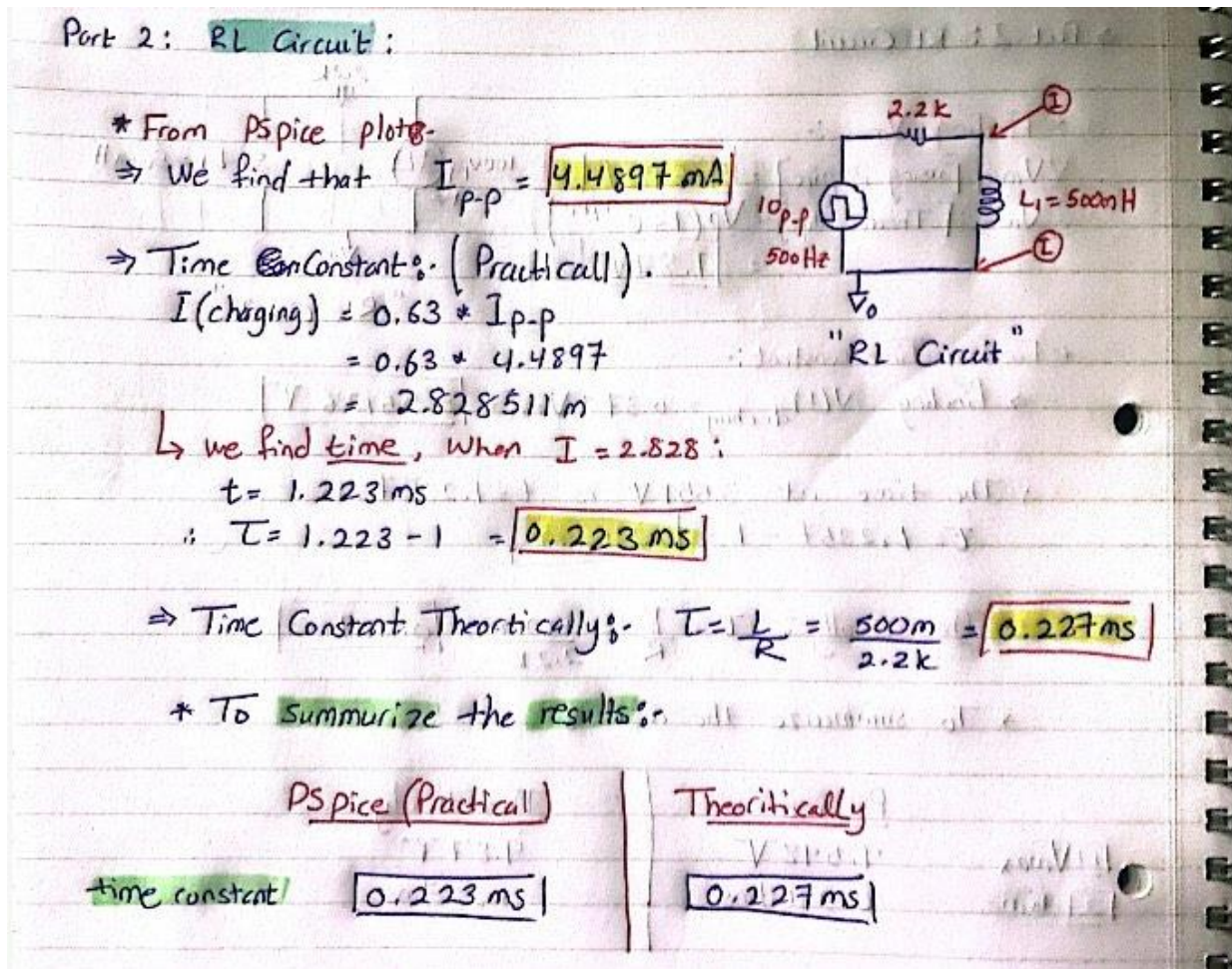


Fig1.10: Time Constant calculations using the plot of the current across the inductor.

- **RL circuit after the period changed to $T=2\tau_L$:**

- ✓ $T = 2 * L/R = 2*(500\text{m}/2.2\text{k}) = 0.454 \text{ msec.}$
- ✓ $F = 1/T = 2.2 \text{ KHz.}$

Which means that:

- ✓ $PER = T = 0.454 \text{ m.}$
- ✓ $PW = \text{pulse width} = 0.5T = 0.5*0.454 = 0.227 \text{ m.}$

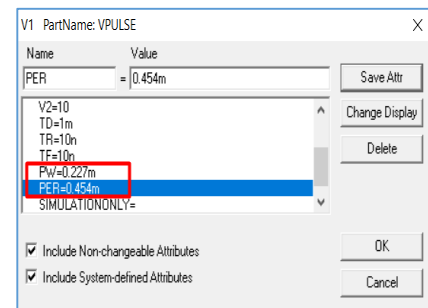


Fig1.11: changing Pulse Voltage settings.

- **Plotting the voltage across the inductor when $T=2\tau L$:**

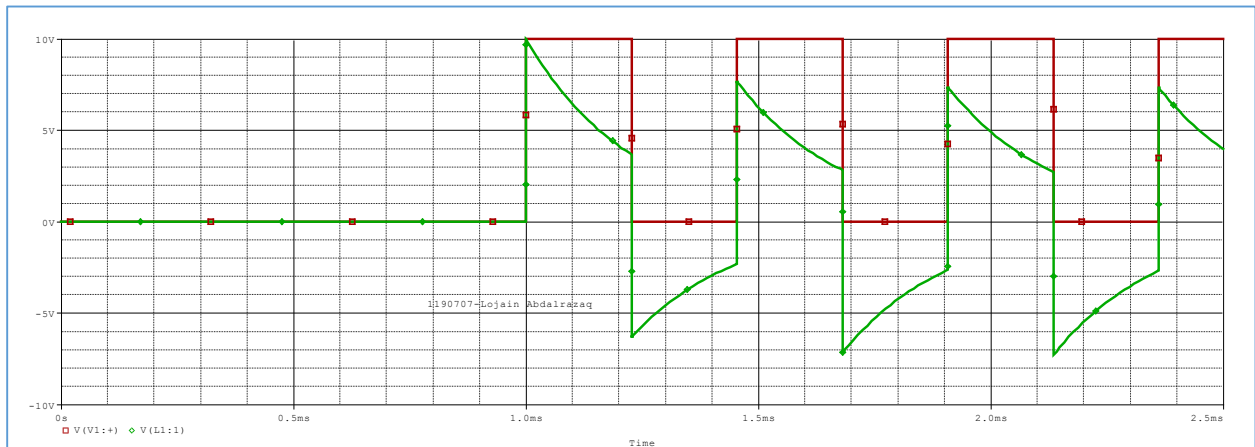


Fig1.12: The voltage response of the inductor when $T=2\tau$.

- **Plotting the current across the inductor when $T=2\tau L$:**

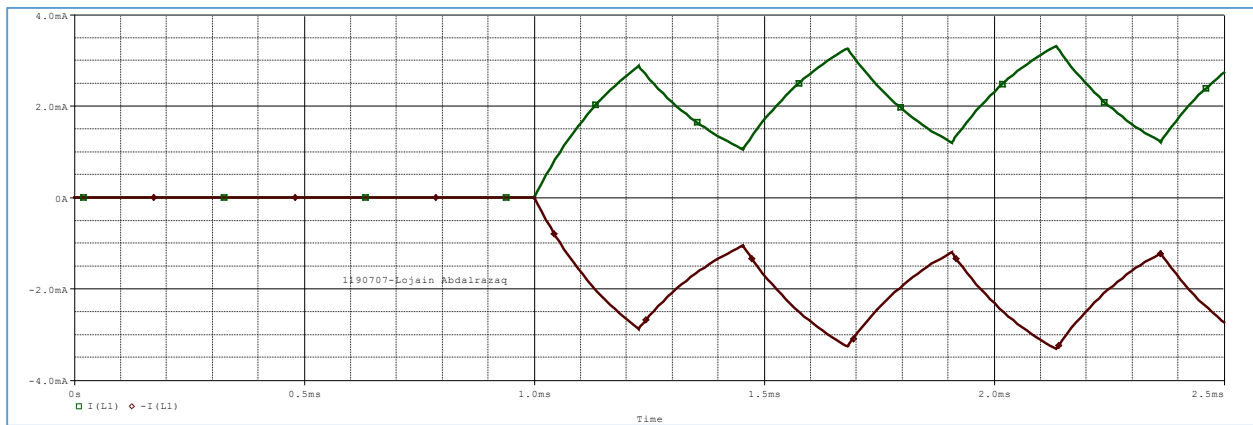


Fig1.13: The current response of the inductor when $T=2\tau$.

3. Part C: RLC Circuit

- **RLC Circuit simulation using PSpice software:**

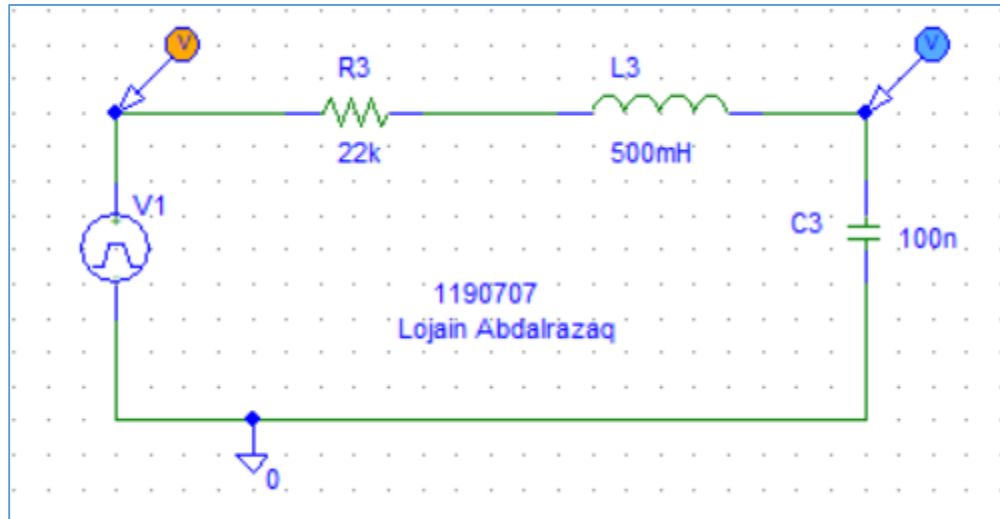


Fig1.14: Circuit simulation using PSpice.

- **Plotting the voltage across the capacitor:**

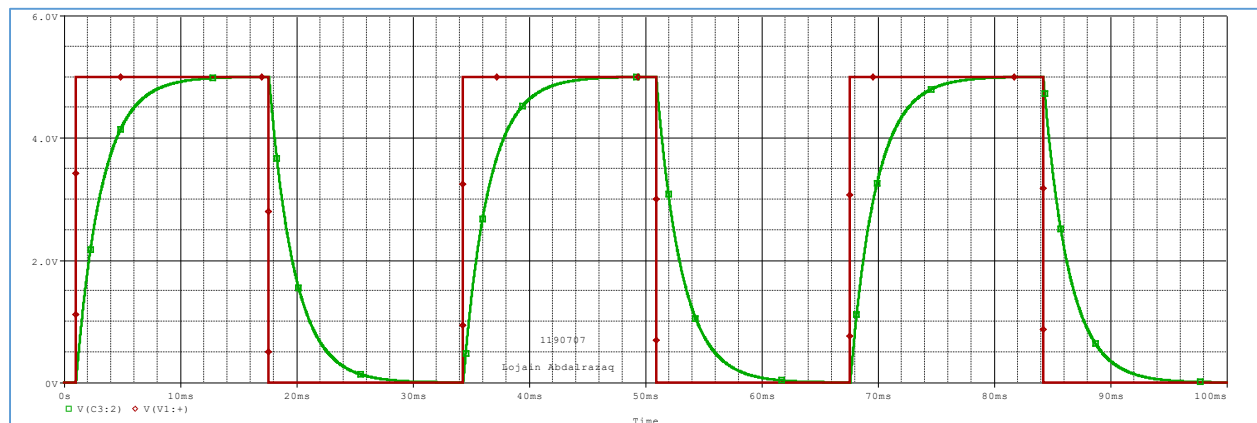


Fig1.15: The voltage response of the capacitor.

✓ Calculating R3 to give critically damped response:

⇒ For damped response case:- $\alpha = \omega_0$

with $\alpha = \frac{R}{2L}$ and $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\therefore \frac{R}{2L} = \frac{1}{\sqrt{LC}} \quad \therefore R = \frac{2L}{\sqrt{LC}} = \frac{2 * 500m}{\sqrt{500m * 100n}} = 4.472.3$$

$$\therefore R = 4.47 \text{ k}\Omega$$

Fig1.16: Finding R3 in critically damped case.

✓ Plotting the voltage across the capacitor when R3=4.47k:


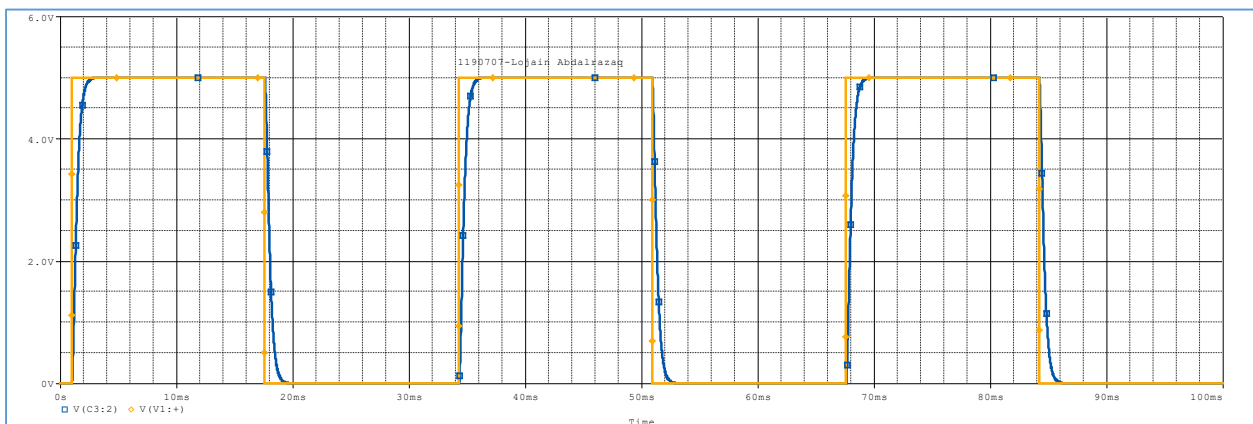


Fig1.17: Voltage across the capacitor when R3=4.47k.

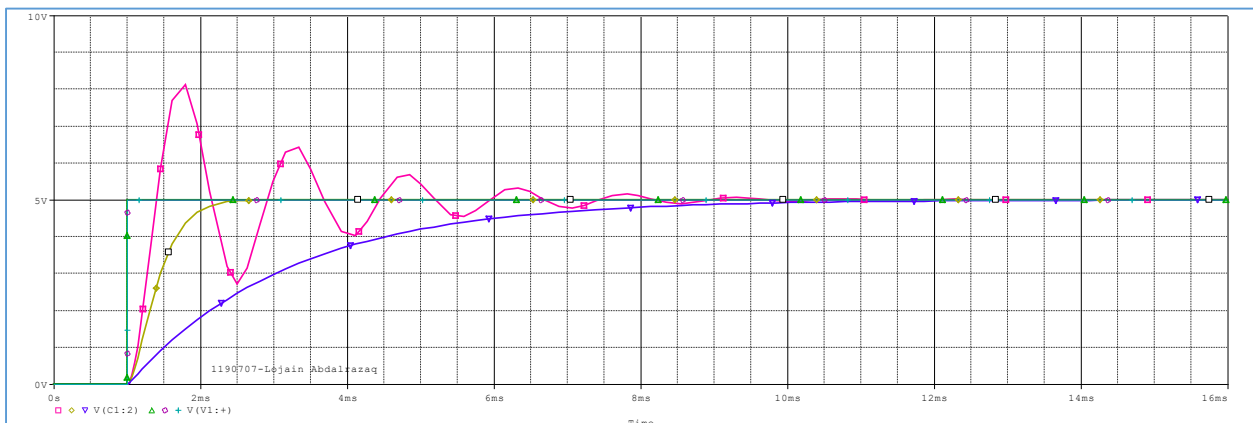✓ Run parametric + transient analysis with varying R3 with 3 values:



✓ Fig1.18: Voltage across the capacitor when R3 varying.

Note:

When $R=4.47k$ which is Critical Damping the output voltage is close to the input one.

- Response parameters:

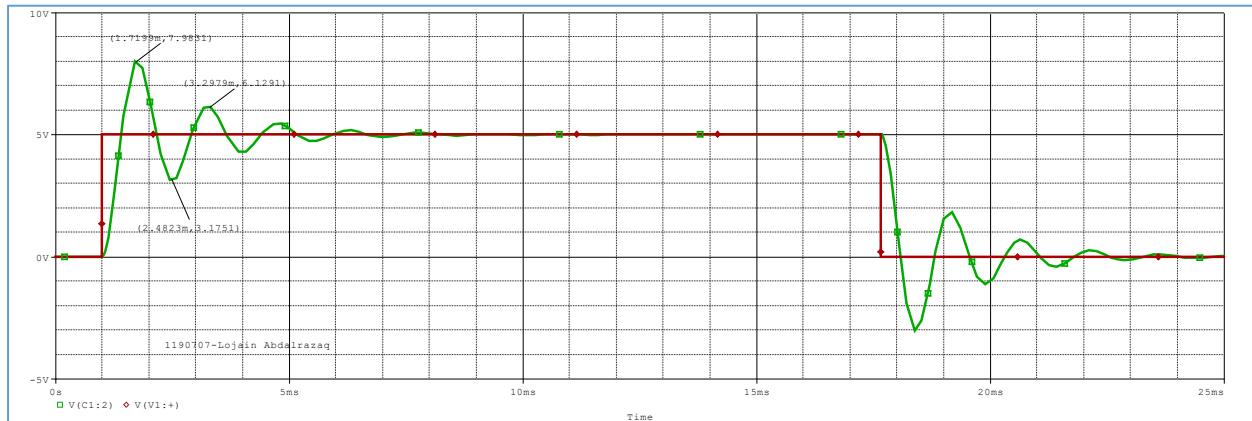


Fig1.19: Response Parameter when $R=750$.

* From the graph, we can find the following:-

$-V_a = 7.9831 \text{ V}$ $-V_b = 6.129 \text{ V}$ Note: $V_o(\infty) = 5 \text{ V}$

$-t_a = 1.7199 \text{ ms}$ $-t_b = 3.2927 \text{ ms}$

$\Rightarrow T = \frac{t_b - t_a}{\ln\left(\frac{V_a - V_o(\infty)}{V_b - V_o(\infty)}\right)} = \frac{3.29 - 1.7199}{\ln\left(\frac{7.98 - 5}{6.129 - 5}\right)} = \frac{1.5728}{\ln(2.639)} = 1.62 \text{ ms}$

$\Rightarrow \text{damping coefficient} = \alpha = \frac{1}{T} = 0.617 \text{ rad/sec}$ (wd)

$\Rightarrow \text{damping radian frequency} = \omega = \frac{1}{\sqrt{LC}} = 4.5 \text{ krad/sec}$ (wd)

$\Rightarrow \text{damping radian frequency} = \omega = \frac{2\pi}{t_b - t_a} = 4 \text{ krad/sec}$ (graph)